

PROBLEM 1 - FULL ADDER

A.

1. @ Using The truth table;

$$S_0 = \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + ABC_i$$

$$S_0 = \bar{A}\bar{B}C_i + ABC_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i$$

$$S_0 = C_i(\bar{A}\bar{B} + AB) + \bar{C}_i(\bar{A}B + A\bar{B})$$


$$S_0 = C_i(A \oplus B) + \bar{C}_i(A \oplus B)$$

$$S_0 = A \oplus B \oplus C_i$$

Using the truth table;

$$C_0 = (A \cdot B) + [(A + B) C_i]$$

B.

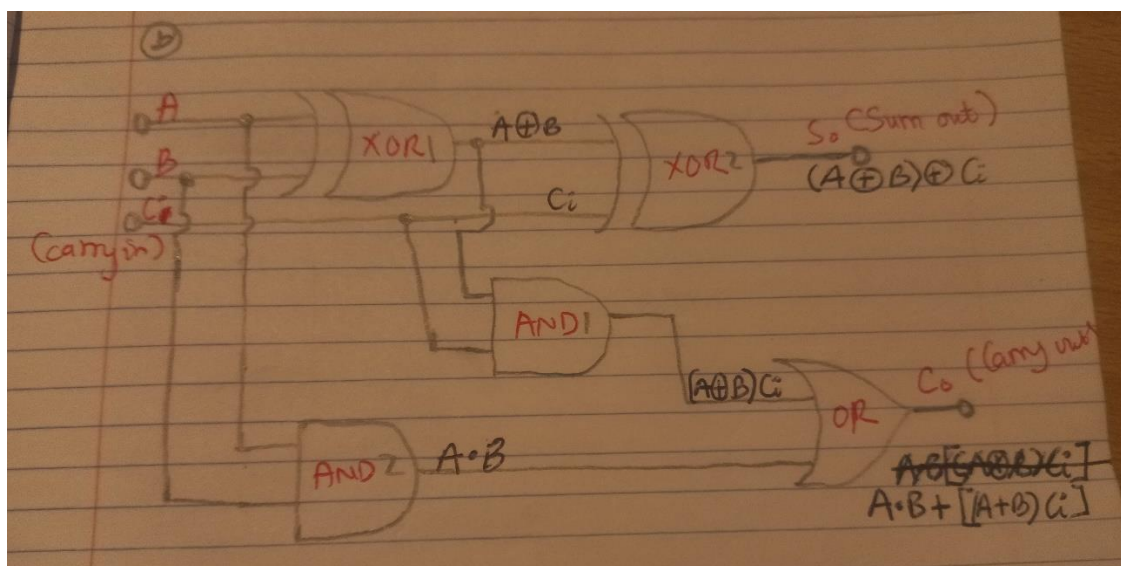

C.

```
`timescale 1ps/1fs

module XORX1 (A, B, C);
    input A, B;
    output C;
    assign C = A ^ B ;
endmodule

module ANDX1 (A, B, C);
    input A, B;
    output C;
    assign C = A & B ;
endmodule

module ORX1 (A, B, C);
    input A, B;
    output C;
    assign C = A | B ;
endmodule

module Cout (A, B, Ci, Co);
    input A, B, Ci;
    output Co;
    logic x1, x2 , x3, x4 ;
    ANDX1 and1 (A, B, x1);
    ANDX1 and2 (A, Ci, x2);
    ANDX1 and3 (B, Ci, x3);
    ORX1 or1 (x1, x2, x4);
    ORX1 or2 (x4, x3, Co);
endmodule

module Sout (A, B, Ci, So);
    input A, B, Ci;
    output So;
    logic x1;
    XORX1 xor1 (A, B, x1 );
    XORX1 xor2 (Ci, x1, So);
endmodule

module fulladder (A, B, Ci, Co, So);
    input A, B, Ci;
```

```

output Co, So;

Cout CO (A, B, Ci, Co);
Sout SO ( A, B, Ci, So);

specify
(A, B, Ci => Co) = (500, 781);
(A, B, Ci => So) = (245, 237);
endspecify

endmodule

```

D. TESTBENCH WITH PLOT SHOWING ALL POSSIBLE SCENARIOS($2^3=8$)


```

`timescale 1ns/1ps
module fulladder_tb();
logic A,B,Ci,Co,So;

fulladder DUT (A,B,Ci,Co,So);

initial begin
    A = 0; B = 0 ; Ci = 0; # 10;
    A = 0; B = 0 ; Ci = 1; # 10;
    A = 0; B = 1 ; Ci = 0; # 10;
    A = 0; B = 1 ; Ci = 1; # 10;
    A = 1; B = 0 ; Ci = 0; # 10;
    A = 1; B = 0 ; Ci = 1; # 10;
    A = 1; B = 1 ; Ci = 0; # 10;
    A = 1; B = 1 ; Ci = 1; # 10;
end
endmodule

```

 

PROBLEM 2 - STATE MACHINE

A. The FSM is a Mealy Machine. The output of each state is dependent on the input(w) of the FSM and the current state.

B.

```
`timescale 1ns/1ps

module MealyMachine (
    input logic clock,
    input logic reset,
    input logic w,
    output logic out
);
    typedef enum logic [2:0] { A, B, C, D, E } state;
    state c_state , n_state ;
    always_ff @( c_state, w ) begin
        case (c_state)
            A : if (w) n_state = B;
                else n_state = A ;
            B : if (w) n_state = C;
                else n_state = A ;
            C : if (w) n_state = D;
                else n_state = A;
            D : if (w) n_state = E;
                else n_state = A;
            E : if (w) n_state = E;
                else n_state = A;
            default: n_state = A;
        endcase
    end
    always_ff @( posedge clock ) begin
        if (reset) c_state = A ;
        else c_state = n_state ;
    end
    assign out = (c_state == A | c_state == E);
endmodule
```

C.

```
`timescale 1ns/1ps
module MealyMachine_tb ();

logic w, clock, reset, out;

MealyMachine DUT (
    .w(w),
    .clock(clock),
    .reset(reset),
    .out(out)
);

initial
    clock = 1'b0;
always #5
    clock = ~clock;

initial begin
    w = 1'b0 ; #20;
    reset = 1'b1 ;#20;
    reset = 1'b0 ;#40;
    w = 1'b1 ;#30;
    w = 1'b1 ;#10;
    w = 1'b0 ;#30;
    w = 1'b1 ;#40;
    w = 1'b1 ;#25;
    $finish();
end
endmodule
```

